Technical Note SIGM20-002


www.signatrak.co.uk

Switching power from the SIGM20 using an RLY2 Relay Board

As the SIGM20 is designed to operate low voltage LED's, devices with higher power consumption require a relay to switch power from the SIGM20.

GFB Designs can supply the RLY2 board which serves this purpose and should be wired as indicated below. This setup will switch the 12V power ON when the "signal" is set to RED and OFF when the "signal" is GREEN.

Wiring Diagram

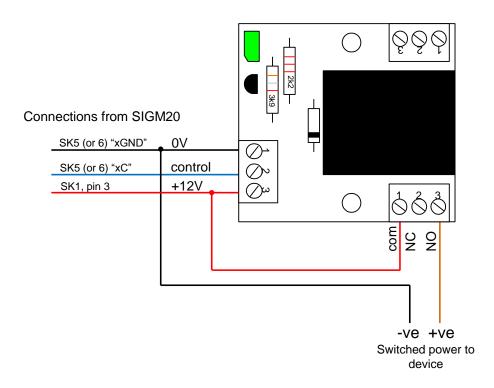

Notes:-

- "x", in the SIGM20 connections list, refers to your i) chosen output (signal) number – i.e. 1 to 4 on SK5 or 5 to 8 on SK6.
- The SIGM20 should be programmed to drive a ii) 2-aspect, common cathode signal.
- iii) Individual wire colours shown to aid clarification only.

Relay contacts:-

Sig-naTrak® by GFB Designs

com Common Normally Closed NC NO Normally Open